

IN1006 Systems Architecture (PRD1 A 2022/23)

[Home](#) | [My Moodle](#) | [IN1006_PRD1_A_2022-23](#) | [COURSEWORK 1: Weekly Assessed Quiz](#) | [Quiz 3_Weekly Assessed Quiz 2022](#)

Started on Thursday, 17 November 2022, 3:45 PM

State Finished

Completed on Thursday, 17 November 2022, 4:00 PM

Time taken 14 mins 45 secs

Grade 10.00 out of 10.00 (100%)

Question 1

Correct

Mark 1.00 out of 1.00

Which of the following statements is *the most accurate* description for the sum-of-products expression below?

$$F = A'BC + ABC' + AB'C'$$


Select one:

- ☐ a. The truth table has three rows where $F = 1$ and no zeros need to be in the inputs to return one.
- ☐ b. The truth table has three rows where $F = 1$ and B must be one to return one.
- ☒ c. The truth table has three rows where $F = 1$ and at least one zero must be in the inputs to return one. ✓
- ☐ d. The truth table has four rows where $F = 1$ and no zeros need to be in the inputs to return one.
- ☐ e. The truth table has two rows where $F = 1$ and no zeros need to be in the inputs to return one.
- ☐ f. Don't know/no answer.

The number of OR-ed terms above specifies the number of input cases that lead to a true expression (rows of truth table that give $F = 1$). Each of the inverted variables shows where the input needs to be zero for that input case.

The correct answer is: The truth table has three rows where $F = 1$ and at least one zero must be in the inputs to return one.

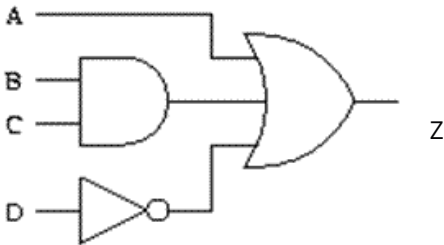Given the logic circuit and table below, which line of the table does *not* correspond with the behaviour of the logic circuit (with output Z)?



Row	A	B	C	D	Z
1	0	0	0	0	1
2	0	0	0	1	0
3	0	0	1	0	1
4	0	0	1	1	0
5	0	1	0	0	1
6	0	1	0	1	0
7	0	1	1	0	1
8	0	1	1	1	1
9	1	0	0	0	1
10	1	0	0	1	1
11	1	0	1	0	1
12	1	0	1	1	1
13	1	1	0	0	1
14	1	1	0	1	1
15	1	1	1	0	0
16	1	1	1	1	1

Select one:

- ☐ a. Row 11
- ☐ b. Row 6
- ☐ c. Row 13
- ☒ d. Row 15
- ☐ e. Row 1
- ☐ f. Row 7
- ☐ g. Don't know/no answer
- ☐ h. Row 3
- ☐ i. Row 10



Row 15 is in error as since A is an input to the final OR-gate and Z should be one when A is one.
The correct answer is: Row 15

Question 3

Correct

Mark 1.00 out of 1.00

Which of the following equations correctly reflects the truth table shown below? A, B and C are inputs and F is the output.

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Select one:

- ☐ a. $F = (A'B'C + A'BC' + AB'C + A'B'C + ABC)'$
- ☒ b. $F = A'B'C + A'BC' + AB'C + ABC$
- ☐ c. $F = A'B'C' + A'BC + AB'C' + ABC'$
- ☐ d. None of these expressions
- ☐ e. Don't know/no answer
- ☐ f. $F = A'B'C' + A'B'C + AB'C' + ABC'$



Your answer is correct.

The F output is given as a sum-of-products expression where each product (AND) should correspond to a row where F = 1.

The correct answer is: $F = A'B'C + A'BC' + AB'C + ABC$

Question 4

Correct

Mark 1.00 out of 1.00

Which of the following equations correctly reflects the truth table shown below? A,B and C are inputs and F is the output.

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Select one:

- ☒ a. $F = A'BC' + A'BC + AB'C' + ABC' + ABC$
- ☐ b. None of these expressions
- ☐ c. $F = (AB'C + A'BC' + A'BC' + A'B'C + A'B'C)'$
- ☐ d. Don't know/no answer
- ☐ e. $F = (A'BC' + A'BC + AB'C' + ABC' + ABC)'$
- ☐ f. $F = AB'C + A'BC' + A'BC' + A'B'C + A'B'C'$



The F output is given as a sum-of-products expression where each product (AND) should correspond to a row where F = 1.


The correct answer is: $F = A'BC' + A'BC + AB'C' + ABC' + ABC$

Question 5

Correct

Mark 1.00 out of 1.00

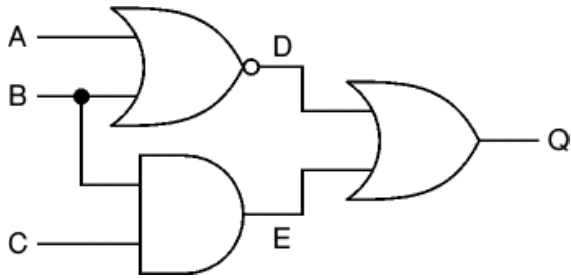Which of the following is the correct Boolean expression for the logic circuit below (with output Q).



Select one:

- ☐ a. $Q = (AB)' + (B+C)$
- ☐ b. $Q = (A+B) + (BC)$
- ☒ c. $Q = (A+B)' + (BC)$
- ☐ d. $Q = (A+B)'(BC)$
- ☐ e. Don't know/no answer



Output Q is OR of a NOR-gate (D) with inputs A, B and an AND-gate (E) with inputs B, C. This gives the expression:

$$Q = (A+B)' + (BC)$$

The correct answer is: $Q = (A+B)' + (BC)$

Question 6

Correct

Mark 1.00 out of 1.00

What is the effect of a bitwise-XOR operation on the following 12-bit words: 1000 1010 1101, 0110 1110 0101?

Select one:


- ☐ a. 0000 1100 0101
- ☒ b. 1110 0100 1000
- ☐ c. 0001 0001 0010
- ☐ d. 1111 0011 1010
- ☐ e. 1110 1110 1101
- ☐ f. Don't know/no answer



The XOR operation is applied to each of the pairs of bits at the same position in each word, moving from left to right.

The correct answer is: 1110 0100 1000

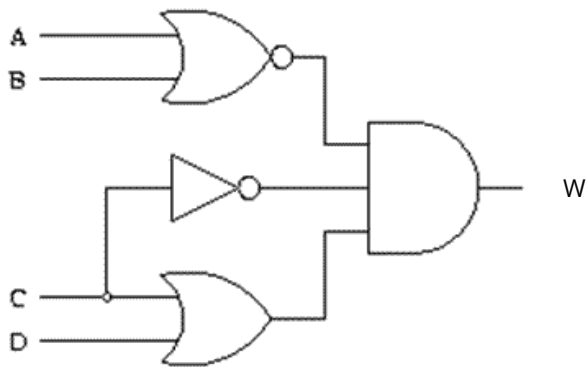Given the logic circuit (with output W) and table below, which line of the table does *not* correspond with the behaviour of the logic circuit?



Row	A	B	C	D	Z
1	0	0	0	0	0
2	0	0	0	1	1
3	0	0	1	0	0
4	0	0	1	1	0
5	0	1	0	0	0
6	0	1	0	1	0
7	0	1	1	0	0
8	0	1	1	1	1
9	1	0	0	0	0
10	1	0	0	1	0
11	1	0	1	0	0
12	1	0	1	1	0
13	1	1	0	0	0
14	1	1	0	1	0
15	1	1	1	0	0
16	1	1	1	1	0

Select one:

- ☐ a. Row 3
- ☐ b. Row 5
- ☐ c. Row 10
- ☒ d. Row 8
- ☐ e. Row 15
- ☐ f. Don't know/no answer
- ☐ g. Row 12
- ☐ h. Row 1
- ☐ i. Row 7



Row 8 is in error as all inputs to the AND gate must be one for W to be one, and this only occurs when the conditions in row two are met.


The correct answer is: Row 8

Question 8

Correct

Mark 1.00 out of 1.00

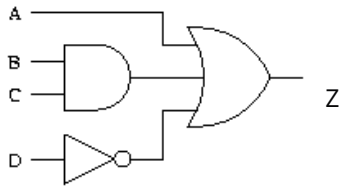Which of the following is the correct Boolean expression for the logic circuit below (with output Z).



Select one:

- ☒ a. $Z = A + (BC) + D'$
- ☐ b. Don't know/no answer
- ☐ c. $Z = A + (B+C)D'$
- ☐ d. $Z = A' + (BC) + D'$
- ☐ e. $Z = A + (BC) + D$



Input D feeds directly into a NOT gate so is inverted to D' . Inputs B and C are AND-ed together. Then all are OR-ed together with A to give the expression:

$$Z = A + (BC) + D'$$

The correct answer is: $Z = A + (BC) + D'$

Question 9

Correct

Mark 1.00 out of 1.00

What is the effect of a bitwise-NAND operation on the following two 12-bit words: 1000 1010 1101, 0110 1110 0101 ?

Select one:


- ☐ a. 0000 1100 0101
- ☒ b. 1111 0101 1010
- ☐ c. 0001 0001 0010
- ☐ d. 1110 0100 1000
- ☐ e. 1110 1110 1101
- ☐ f. Don't know/no answer



The NAND operation is applied to each of the pairs of bits at the same position in each word, moving from left to right.

The correct answer is: 1111 0101 1010

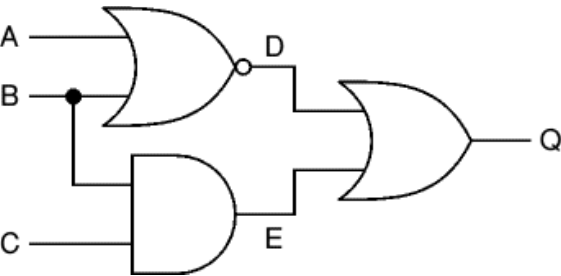Given the logic circuit and table below (with output Q), which line of the table does *not* correspond to the behaviour of the logic circuit?



Row	A	B	C	Q
1	0	0	0	1
2	0	0	1	1
3	0	1	0	1
4	0	1	1	1
5	1	0	0	0
6	1	0	1	0
7	1	1	0	0
8	1	1	1	1

Select one:

- ☐ a. Row 8
- ☐ b. Don't know/no answer
- ☐ c. All rows are correct
- ☐ d. Row 7
- ☐ e. Row 5
- ☐ f. Row 2
- ☐ g. Row 4
- ☐ h. Row 1
- ☒ i. Row 3
- ☐ j. Row 6



Row 3 is in error as the output of the NOR-gate (D) and AND-gate (E) are zero, leading to an output of the OR-gate (Q) of zero.

The correct answer is: Row 3

1	2	3	4	5	6	7	8	9	10
---	---	---	---	---	---	---	---	---	----

[Show one page at a time](#)

[Finish review](#)